




HIGH VOLTAGE MEASUREMENT BRIDGE CIRCUIT

THT10KV V2.0

Translator : jeromero (Jérôme)

Working with High Voltage electrical values leads us against the difficulty of measurement.

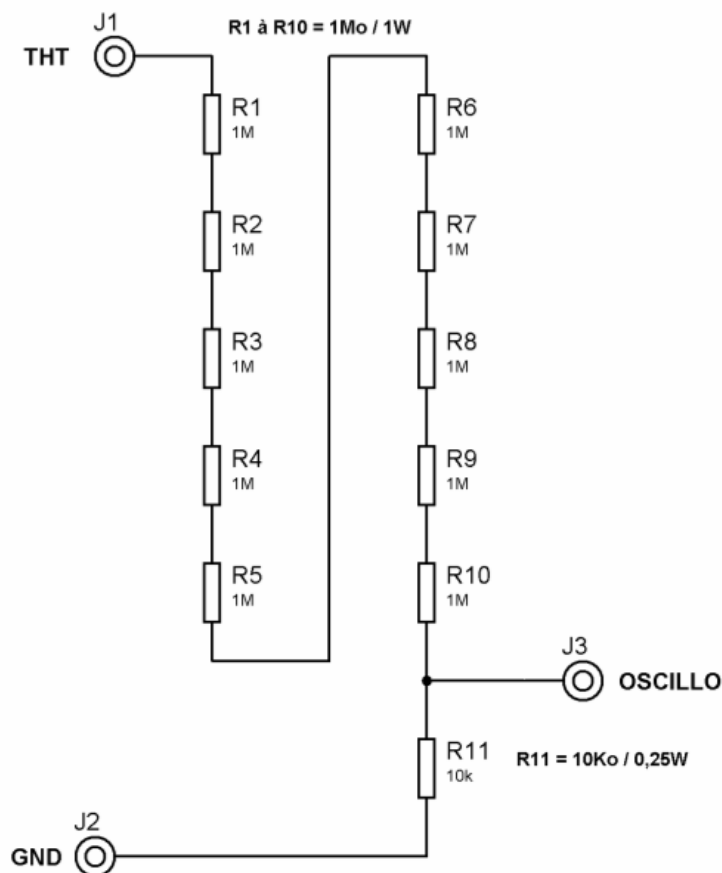Unless using a specific measuring device, the only way to realize this measure requires a divisor bridge circuit :



Simple, easy to realize and cheap, it doesn't bring commercial divisor bridge accuracy.

Maximum Input Voltage : 10 kV


Amperage (10 kV input) : 1mA (strong enough !)

Scale : **1V/kV**

Accurately, according to the error generated by the resistance values and their tolerances (that's why we advice you to choose resistors 1%), with 10kV input voltage, you will measure an output voltage of 9.99v (instead of 10v).

Making

Simple sided PCB 5,11" x 3,94" :

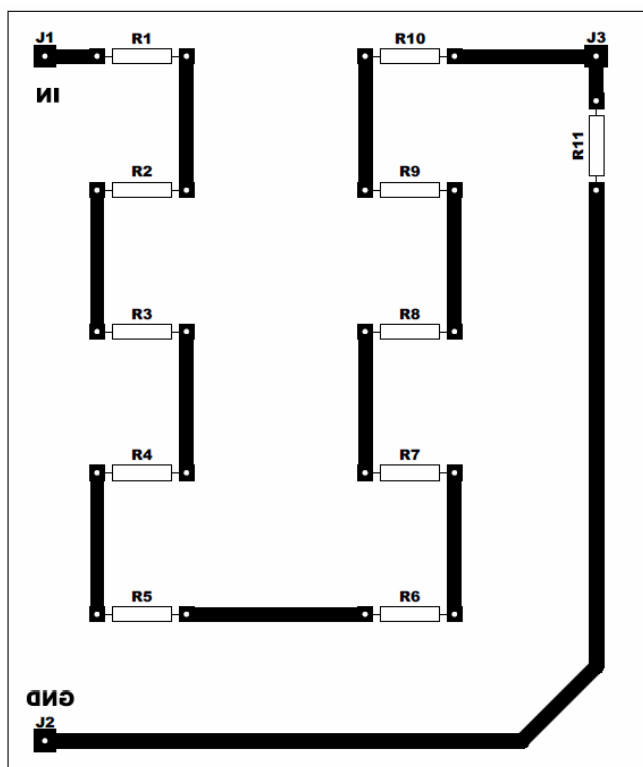

Once realized, fill both side (except input/output pins) with glu.

WARNING: Use only 10 pieces of 1M Ω / 1W resistors even if you got a 10M Ω resistor (unless it's a 10W power)

Subject to mistakes or omissions...

On September 27, 2010

 $\mathcal{A}sl$

Terms of use

This document may be freely redistributed, but always in its entirety.

All rights to the content of this document, text and diagrams that come with, remain the exclusive property of *Génération Hydrogène*.

Thus, any partial copy or reproduction is strictly prohibited.

The author will not be held responsible, under no circumstances, due to any direct or indirect consequence resulting from reading and / or applying the concept described in this document.

Any commercial use is prohibited without the agreement of the *Génération Hydrogène* administrator.